

---

# Design of Analog CMOS Integrated Circuits

*<Chapter 4>*

*Differential Amplifiers*

*양병도*

## 4.1 Single-ended vs. Differential Signals



### □ Differential Signals

✓ 장점:

- 잡음에 강하다 → Common mode (CM) noise 제거
- Swing 전압 증가 →  $2 \times [V_{DD} - (V_{GS} - V_{TH})]$
- Bias 쉽고 linearity 증가



✓ 단점:

- 면적/ 전력 증가

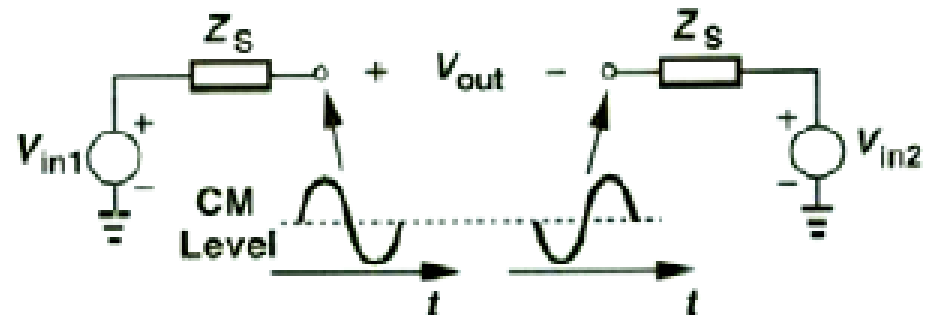
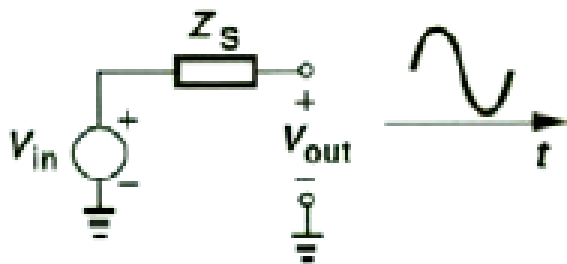


# Advantages of differential operation

## ❑ Reduction of coupling

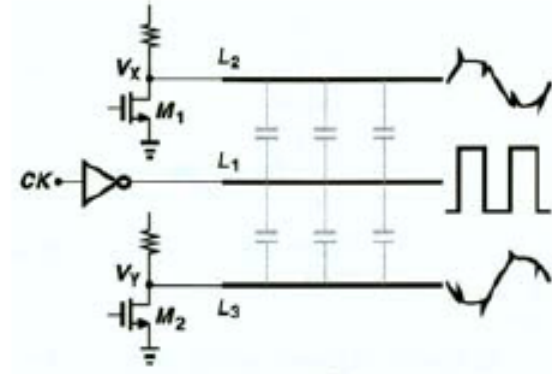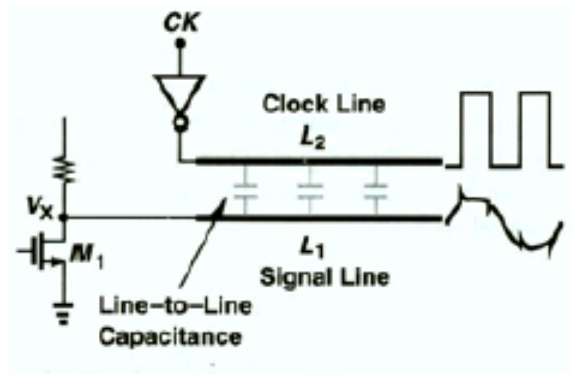

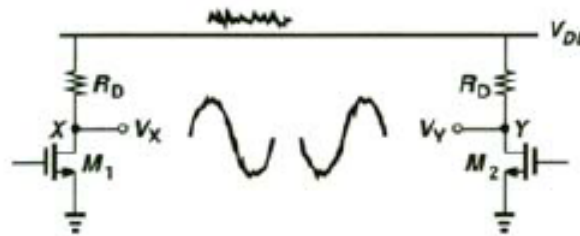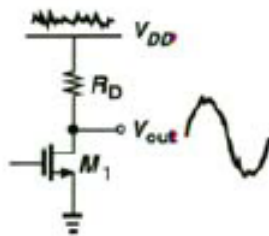
## ❑ Common-mode rejection occurs with noisy supply voltages


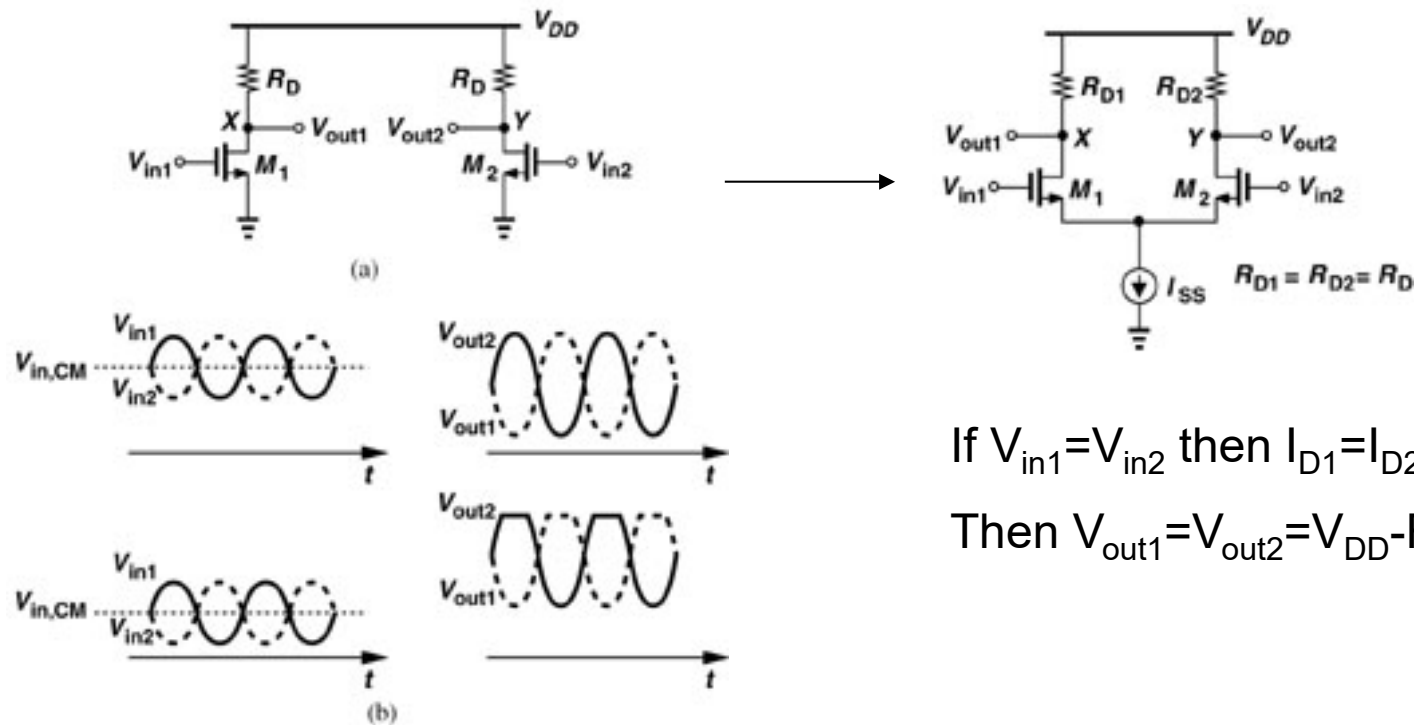
## 4.2 Basic differential pair

- ❑ 문제점:  $v_{in1}$ 과  $v_{in2}$ 의 CM level 변화  $\rightarrow$  bias current 변화  $\rightarrow$  gain 변화
- ❑ 해결: bias current source 사용  $\rightarrow$  CM level 변화  $\rightarrow$  bias current 일정  $\rightarrow$  gain 일정



If  $V_{in1} = V_{in2}$  then  $I_{D1} = I_{D2} = I_{SS}/2$

Then  $V_{out1} = V_{out2} = V_{DD} - R_D I_{SS}/2$

# 정성적 분석

If  $V_{in1} \gg V_{in2}$ ,

M1 off  $\rightarrow V_{out1} = V_{DD}$

M2 on  $\rightarrow I_{SS} \rightarrow V_{out2} = V_{DD} - R_D I_{SS}$




If  $V_{in1} = V_{in2}$

$I_{D1} = I_{D2} = I_{SS}/2$


$V_{out1} = V_{out2} = V_{DD} - R_D I_{SS}/2$

If  $V_{in1} \ll V_{in2}$ ,

첫 번째와 반대

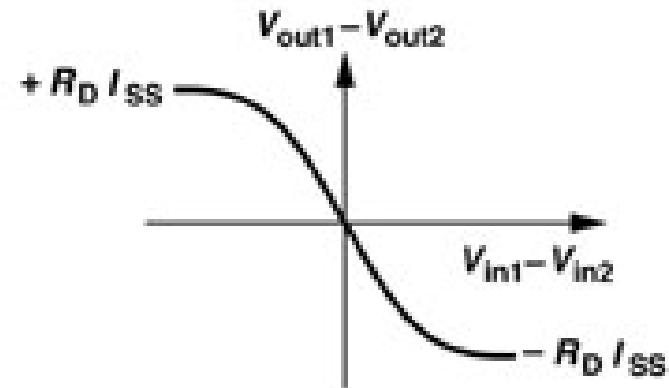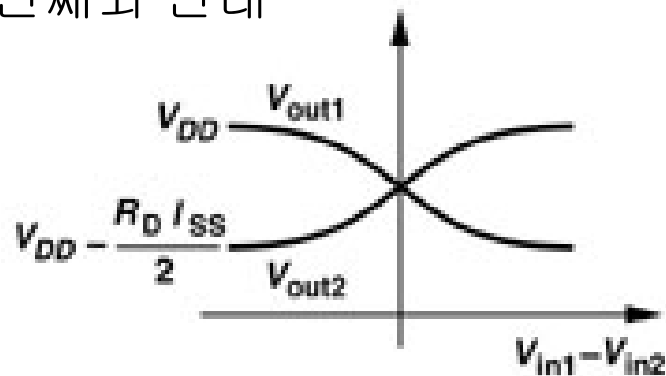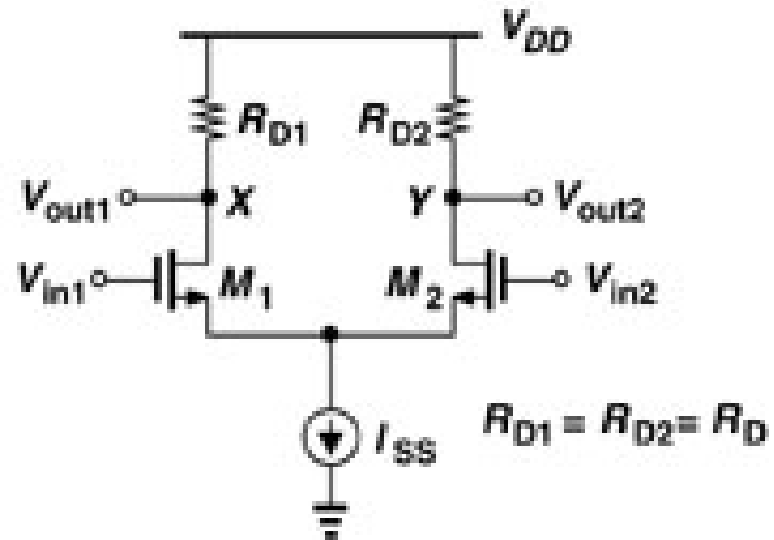

# Common-Mode Response

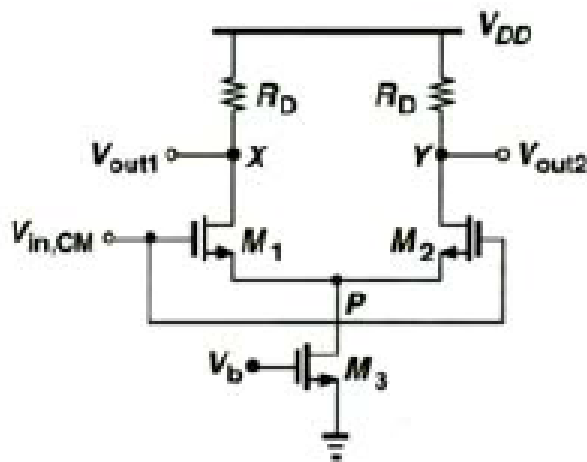

□ M3가 saturation에서 동작

✓  $\rightarrow V_p > V_{GS3} - V_{TH3}$

✓  $\rightarrow V_{in,CM} > V_{GS1} + (V_{GS3} - V_{TH3})$

□ M1이 saturation에서 동작


✓  $\rightarrow V_{out1} > V_{in,CM} - V_{TH1}$

✓  $\rightarrow V_{in,CM} < V_{out1} + V_{TH1}$

✓  $= V_{DD} - R_D I_{SS} / 2 + V_{TH1}$

$$V_{GS1} + (V_{GS3} - V_{TH3}) \leq V_{in,CM} \leq \min[V_{DD} - R_D \frac{I_{SS}}{2} + V_{TH1}, V_{DD}]$$

## 정량적 분석(1/3)

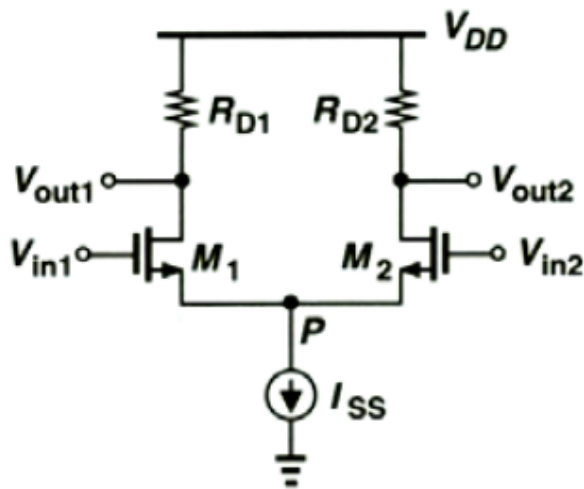

$$V_{out1} = V_{DD} - R_{D1}I_{D1} \quad , \quad V_{out2} = V_{DD} - R_{D2}I_{D2}$$

$$[R_{D1} = R_{D2} = R_D]$$

$$\Rightarrow V_{out1} - V_{out2} = R_{D2}I_{D2} - R_{D1}I_{D1} = R_D (I_{D2} - I_{D1})$$

Assuming the circuit is symmetric,  $M_1$  and  $M_2$  are saturated, and  $\lambda = 0$ ,

$$V_{in1} - V_{in2} = V_{GS1} - V_{GS2}$$


For a square-law device, we have:

Therefore,

$$V_{in1} - V_{in2} = \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \frac{W}{L}}}$$

Recognizing that  $I_{D2} + I_{D1} = I_{SS}$ , we obtain

## 정량적 분석(2/3)

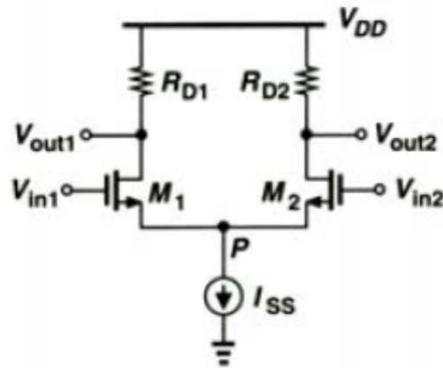

⇒

$$(V_{in1} - V_{in2})^2 = \frac{2}{\mu_n C_{ox} \frac{W}{L}} (I_{SS} - 2\sqrt{I_{D1}I_{D2}})$$

$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 - I_{SS} = -2\sqrt{I_{D1}I_{D2}}$$


Squaring the two sides again and  $4I_{D1}I_{D2} = (I_{D1} + I_{D2})^2 - (I_{D1} - I_{D2})^2 = I_{SS}^2 - (I_{D1} - I_{D2})^2$ ,

we arrive at 
$$I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}$$

Denoting  $\Delta I_D = I_{D1} - I_{D2}$  and  $\Delta V_{in} = V_{in1} - V_{in2}$ , we can show that

$$\frac{\partial \Delta I_D}{\partial \Delta V_{in}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \frac{\frac{4I_{SS}}{\mu_n C_{ox} W/L} - 2\Delta V_{in}^2}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} W/L} - \Delta V_{in}^2}}$$

## 정량적 분석(3/3)


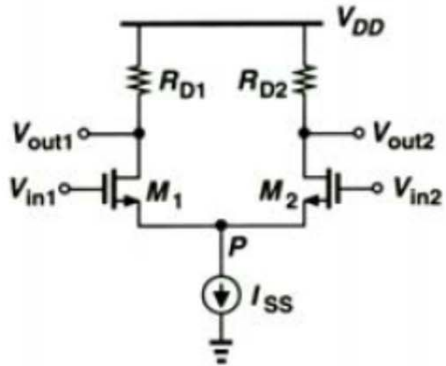


- For  $\Delta V_{in} = 0$ ,  $G_m = \left. \frac{\partial \Delta I_D}{\partial \Delta V_{in}} \right|_{V_{in}=0} = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}}$
- Since  $\Delta V_{out} = V_{out1} - V_{out2} = R_D \Delta I_D = R_D G_M \Delta V_{in}$ , the small-signal differential gain is given as

$$|A_v| = G_m R_D = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} \cdot R_D$$



- $G_M = 0$  for  $\Delta V_{in} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} W / L}}$

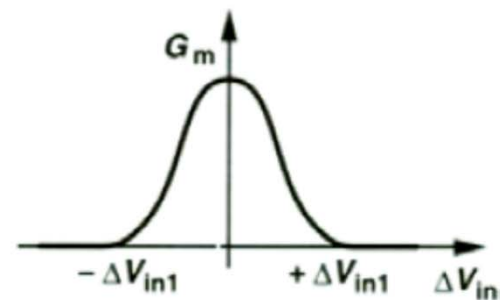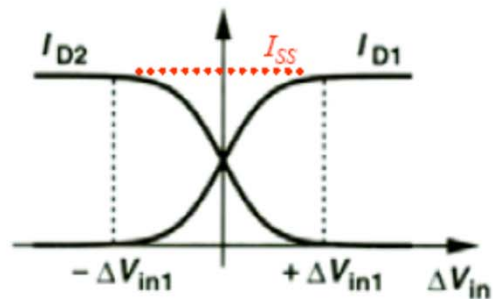Variation of  $I_D$  and  $G_M$  vs.  $\Delta V_{in}$


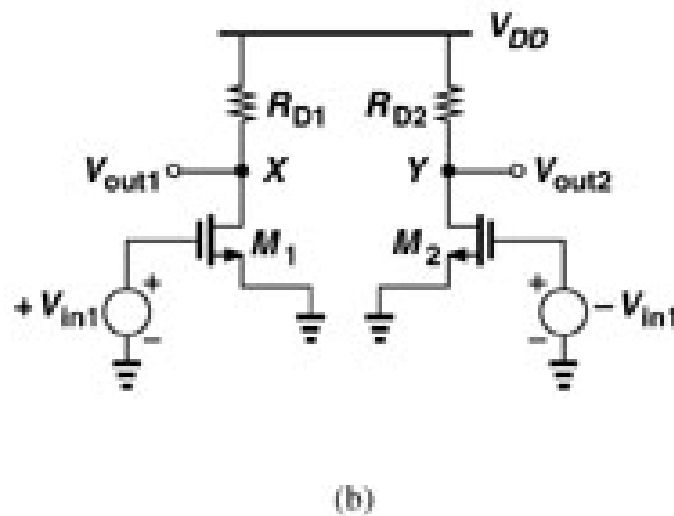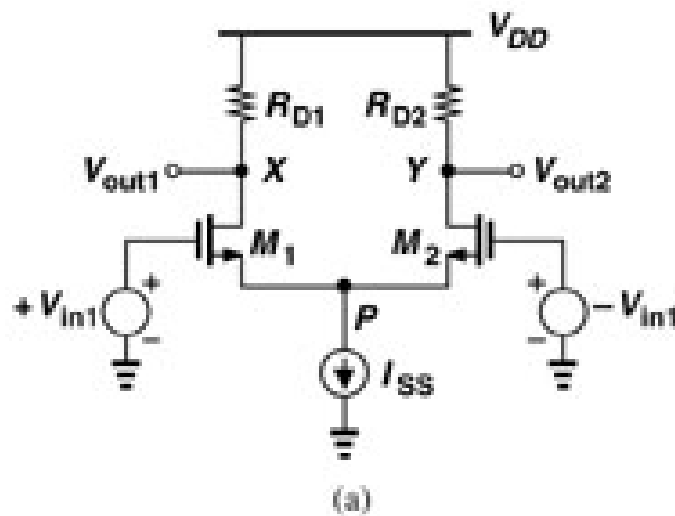
## Small signal 해석 (Half circuit 이용)

- Differential pair가 완전히 symmetric한 경우
- Small signal의 node P를 virtual ground로 본다.
- CS와 같은 방식으로 해석 → 간단해짐




# Small signal 해석 (superposition 이용)

□ (1)  $V_{in2}=0$  일 때



✓ Neglecting  $\lambda_2$  and  $g_{mb2}$   $R_S \approx 1/g_{m2}$

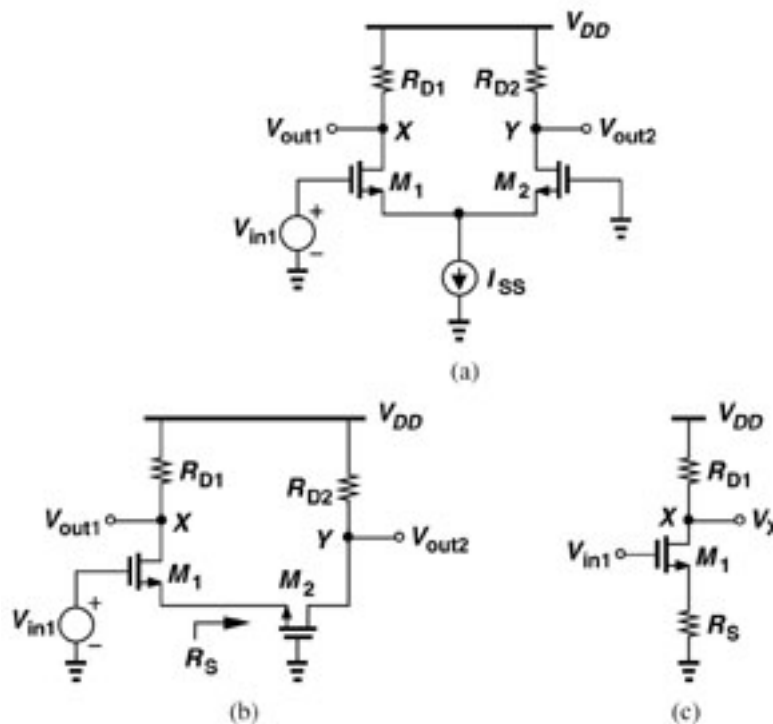□ Differential Gain: Effect of  $V_{in1}$  on  $V_X$



$$\frac{V_X}{V_{in1}} \approx \frac{-R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

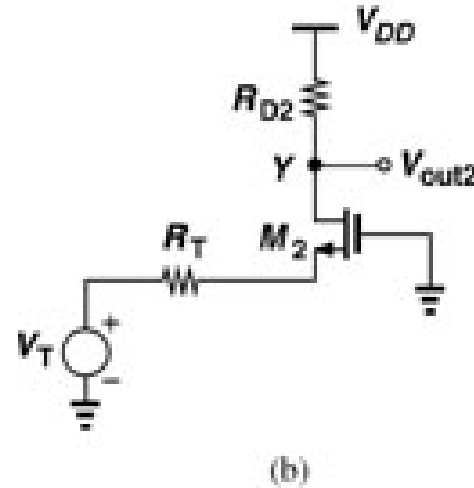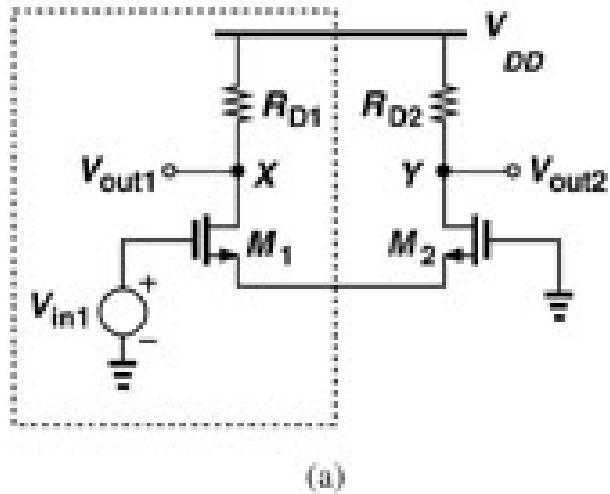□ Differential Gain: Effect of  $V_{in1}$  on  $V_Y$



$$\frac{V_Y}{V_{in1}} \approx \frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

□  $V_X - V_Y$  as function of  $V_{in1}$  if  $V_{in2}=0$

✓  $g_{m1} = g_{m2} = g_m$

$$(V_X - V_Y)_{due\_to\_V_{in1}} = \frac{-2R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} V_{in1} = -g_m R_D V_{in1}$$

□ (2)  $V_{in1}=0$  일 때

□  $V_X - V_Y$  as function of  $V_{in2}$  if  $V_{in1}=0$

$$(V_X - V_Y)_{due\_to\_V_{in2}} = \frac{2R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} V_{in2} = g_m R_D V_{in2}$$


□  $V_X - V_Y$  as function of  $V_{in2}$  and  $V_{in1}$

$$(V_X - V_Y)_{due\_to\_both} = g_m R_D V_{in2} - g_m R_D V_{in1}$$

$$A_v(diff) = \frac{V_{out1} - V_{out2}}{V_{in1} - V_{in2}} = g_m R_D$$


$$A_v(S.E.) = \frac{g_m}{2} R_D$$
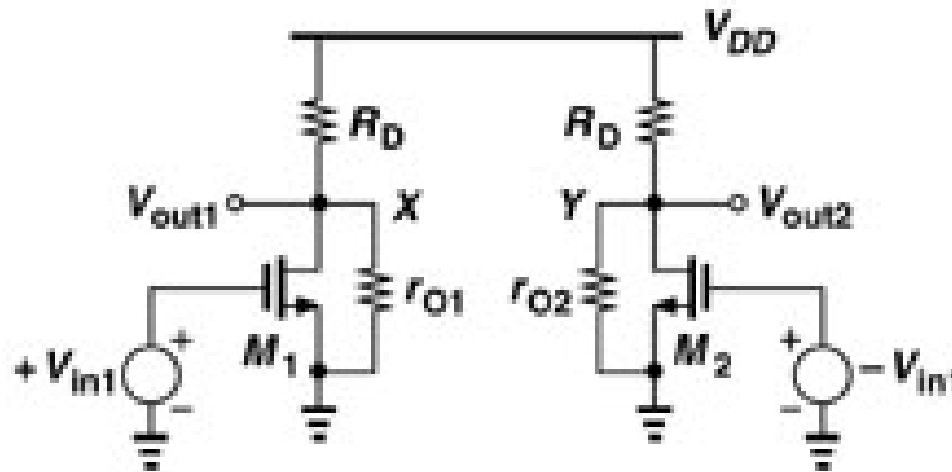
# Differential Gain with $\lambda$ effect



- Based on the half-circuit concept, gain calculation is highly simplified.
- $V_X/V_{in1} = -g_m(R_D \parallel r_o) = V_Y/(-V_{in1})$
- $(V_X - V_Y)/2V_{in1} = -g_m(R_D \parallel r_o)$



## 4.3 Common mode response

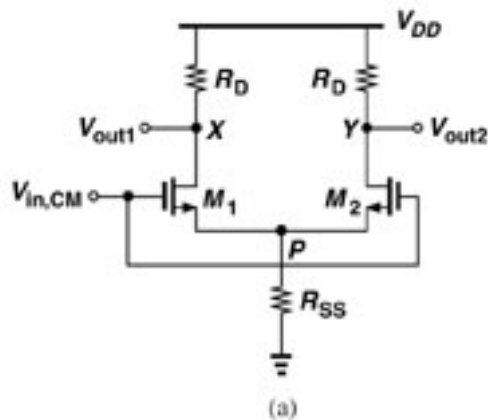


$$A_{V,CM} = \frac{V_{out}}{V_{in,CM}} = \frac{V_X}{V_{in,CM}} = \frac{V_Y}{V_{in,CM}}$$

$$= -\frac{R_D / 2}{1/(2g_m) + R_{SS}}$$

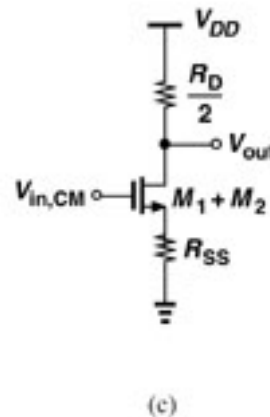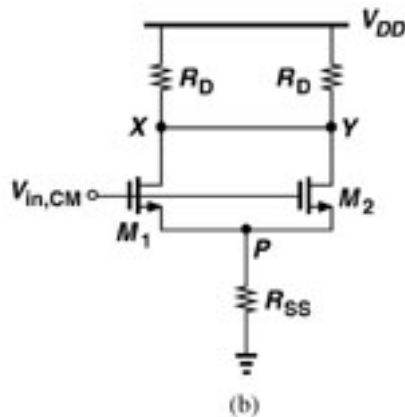$M_1 + M_2$  has twice the width and bias current, therefore  $g_m$  is doubled.


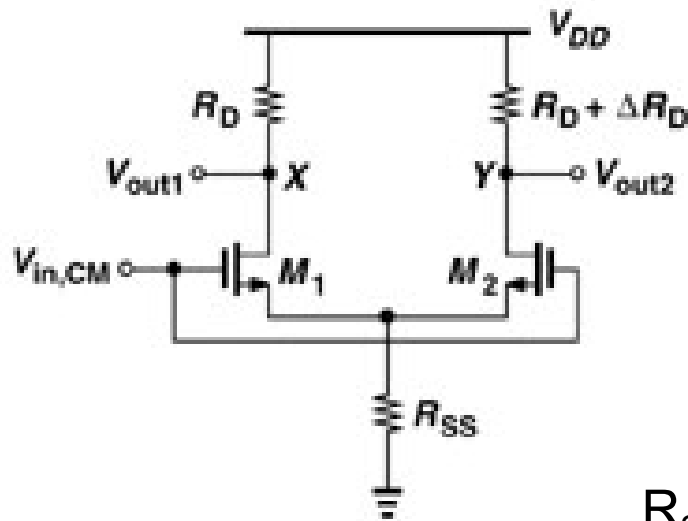
## Common-Mode Response with asymmetric $R_D$ assuming $\lambda=0$





$$\frac{\Delta V_X}{\Delta V_{in,CM}} = -\frac{g_m}{1 + 2g_m R_{SS}} R_D$$

$$\frac{\Delta V_Y}{\Delta V_{in,CM}} = -\frac{g_m}{1 + 2g_m R_{SS}} (R_D + \Delta R_D)$$

$$\frac{\Delta V_X - \Delta V_Y}{\Delta V_{in,CM}} = \frac{g_m}{1 + 2g_m R_{SS}} \Delta R_D$$

$R_{SS}$  above represents the current source  
 $\rightarrow$  need large  $R_{SS}$

## $g_m$ mismatch

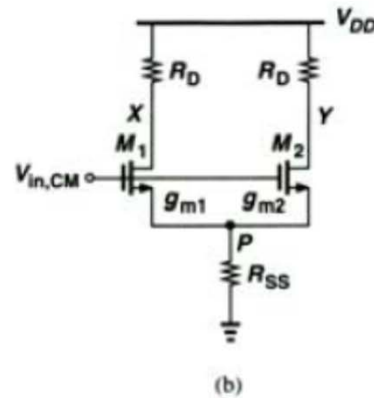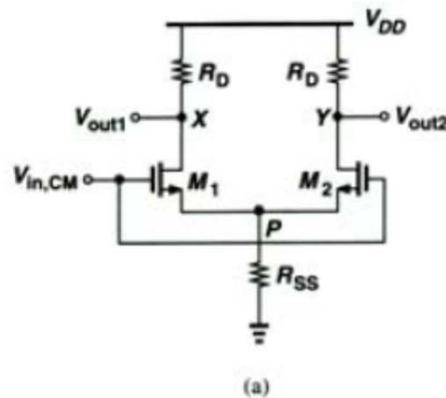

$$\begin{aligned} \begin{cases} I_{D1} = g_{m1}(V_{in,CM} - V_P) \\ I_{D2} = g_{m2}(V_{in,CM} - V_P) \end{cases} \\ \Rightarrow (g_{m1} + g_{m2})(V_{in,CM} - V_P) = V_P / R_{SS} \\ \Rightarrow V_P = \frac{(g_{m1} + g_{m2})R_{SS}}{(g_{m1} + g_{m2})R_{SS} + 1} V_{in,CM} \end{aligned}$$

$$\begin{cases} V_X = -g_{m1}(V_{in,CM} - V_P)R_D = -\frac{g_{m1}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D V_{in,CM} \\ V_Y = -g_{m2}(V_{in,CM} - V_P)R_D = -\frac{g_{m2}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D V_{in,CM} \end{cases} \Rightarrow V_X - V_Y = -\frac{g_{m1} - g_{m2}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D V_{in,CM}$$

Thus, the circuit converts input CM variations to a differential error by a factor equal to



$$A_{CM-DM} = -\frac{\Delta g_m R_D}{(g_{m1} + g_{m2})R_{SS} + 1}$$

$A_{CM-DM}$ : CM to DM conversion

$$\Delta g_m = g_{m1} - g_{m2}$$

# Common-Mode Rejection Ratio (CMRR)

Definition  $CMRR = \left| \frac{A_{DM}}{A_{CM-DM}} \right|$

If only  $g_m$  mismatch is considered

- Differential mode (assume  $V_{in1} = -V_{in2}$ )

$$|A_{DM}| = \frac{R_D}{2} \frac{g_{m1} + g_{m2} + 4g_{m1}g_{m2}R_{SS}}{1 + (g_{m1} + g_{m2})R_{SS}}$$




- Common-mode to differential-mode conversion

$$A_{CM-DM} = -\frac{\Delta g_m R_D}{(g_{m1} + g_{m2})R_{SS} + 1}$$



- CMRR

$$CMRR = \frac{g_{m1} + g_{m2} + 4g_{m1}g_{m2}R_{SS}}{2\Delta g_m}$$
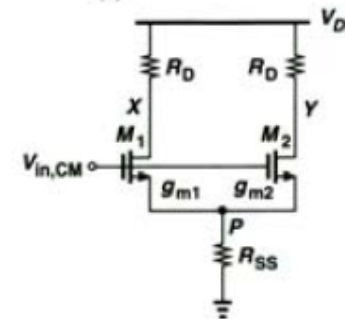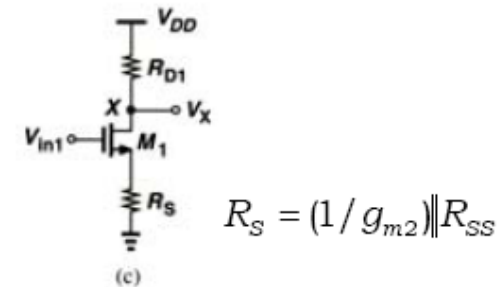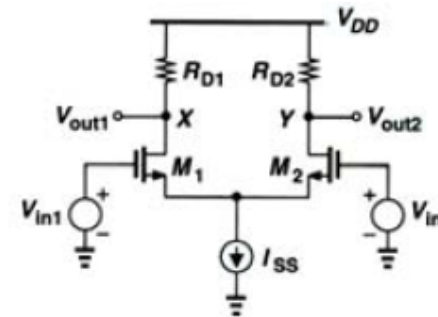
$$\approx \frac{g_m}{\Delta g_m} [1 + 2g_m R_{SS}]$$



## 4.4 Differential pair with MOS Load

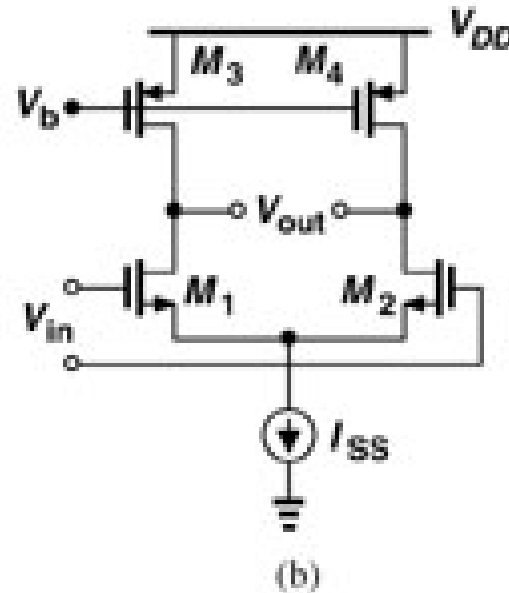
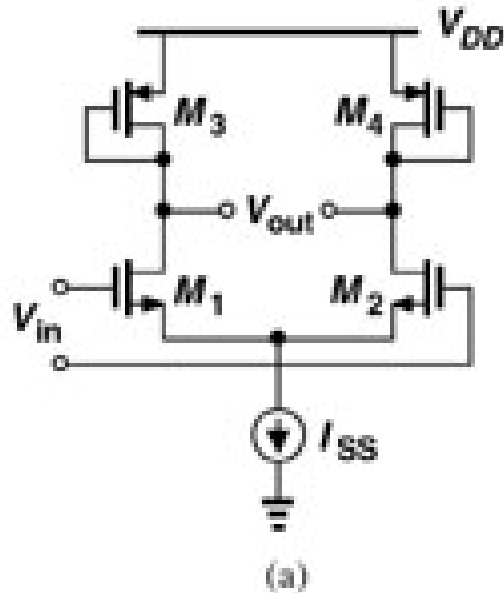


$$A_{V,diff} = -g_{mN} (g_{mP}^{-1} \parallel r_{oN} \parallel r_{oP})$$

$$\approx -\frac{g_{mN}}{g_{mP}} = -\sqrt{\frac{\mu_n (W/L)_N}{\mu_p (W/L)_P}}$$

$$A_{V,diff} = -g_{mN} (r_{oN} \parallel r_{oP})$$
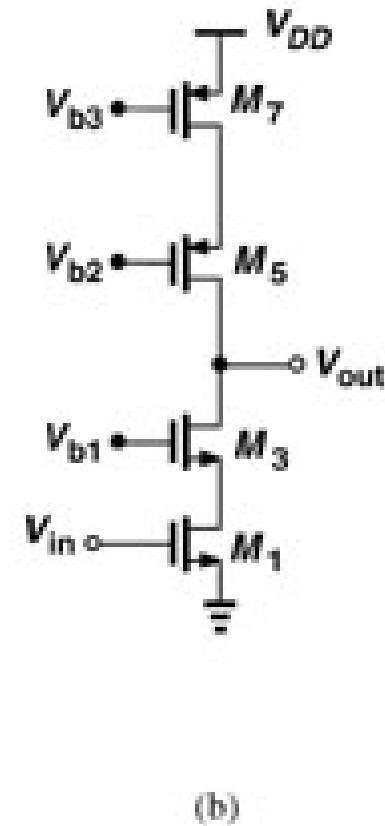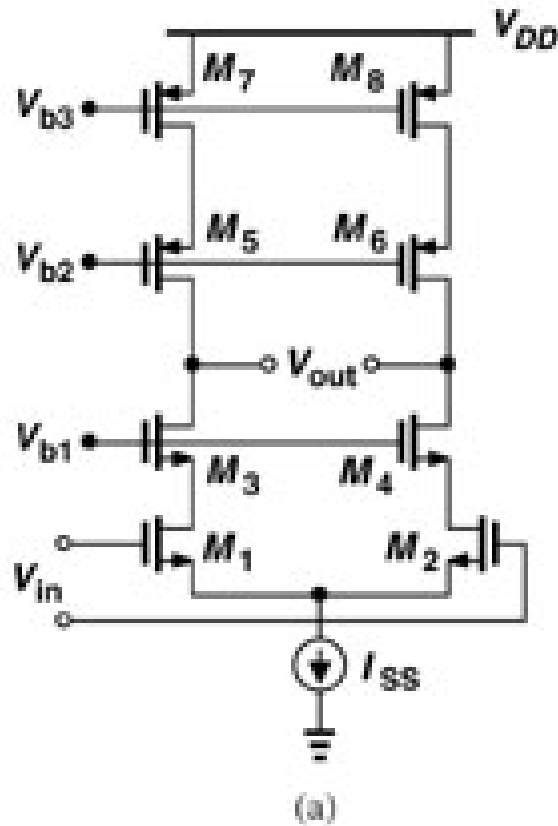
# Solution to low-gain problem: Cascoding



$$A_{V,diff} \approx g_{m1}[(g_{m3}r_{o3}r_{o1}) \parallel (g_{m5}r_{o5}r_{o7})]$$