
Design of Analog CMOS Integrated Circuits

<Chapter 9>

Operational Amplifiers

양병도

9.1 Performance Parameters

□ Gain

- ✓ Open-loop gain은 feedback system에서의 정확도 결정 → High open-loop gain


□ Example 9.1

- ✓ $1 + R_1/R_2 = 10$
- ✓ Error가 1% 미만이기 위한 A_1 ?

$$\frac{V_{out}}{V_{in}} = \frac{A_1}{1 + \frac{R_2}{R_1 + R_2} A_1} = \frac{R_1 + R_2}{R_2} \cdot \frac{A_1}{\frac{R_1 + R_2}{R_2} + A_1}$$


$$\text{If } A_1 \gg (R_1 + R_2)/R_2, \text{ then } \frac{V_{out}}{V_{in}} \approx \left(1 + \frac{R_1}{R_2}\right) \left(1 - \frac{R_1 + R_2}{R_2} \frac{1}{A_1}\right)$$

$$A_1 > 1000.$$

 


□ Simple CS stage – an open-loop implementation:

 - ✓ Error 1% 미만 만들기 어렵다.
- ✓ 왜? → NMOS, 저항 variation → ~20%




$$\left| \frac{V_{out}}{V_{in}} \right| = g_m R_D = 10$$

□ Small-signal bandwidth

 

□ Large-signal bandwidth – slew rate

 

❑ Output swing

- ✓ 대부분의 시스템에서는 output swing 전압이 큰 Op-Amp를 필요로 한다.

❑ Linearity


- ✓ Open-loop op amp 는 non-linearity 영향을 크게 받는다.
- ✓ input pair M_1 - M_2 에서 입력 전압과 drain 전류 사이에 non-linearity가 발생한다.

❑ Noise and offset

- ✓ 입력 노이즈와 offset에 의하여 입력 전압의 최소 전압 수준이 결정된다.


❑ Supply rejection

 - ✓ Digital 전원과 함께 사용하는 전원에 의한 노이즈를 받게 되는데, Op-amp의 성능에서 전원 노이즈를 제거하는 것이 꼭 필요하고, 따라서, differential 회로가 많이 사용된다.




9.2 One-stage op amps

□ Simple op amp

 

Differential input & single-ended output

 

Differential input & differential output

- ✓ Low frequency gain = $gm_N (ro_N \parallel ro_P)$. → submicron devices 에서 20 넘기 힘들다.
- ✓ bandwidth 는 C_L 에 의하여 결정된다.
- ✓ M_1 - M_4 에 의한 노이즈 영향을 받는다.

□ Unit-gain buffer



✓ Input common-mode voltage range

$$V_{in,min} = V_{CSS} + V_{GS1}$$
$$V_{in,max} = V_{DD} - |V_{GS3}| + V_{TH1}$$

- If $V_{TH}=0.7V$ and $V_{ov}=V_{GS}-V_{TH}=0.3V$,
- then $V_{in,min} = 1.3V$ and $V_{in,max} = 2.7V$
- Input CM range = 1.4V with $V_{DD}=3V$

✓ Output impedance
  
$$R_{out} = \frac{R_{out,open}}{1 + \beta A_{v,open}} = \frac{r_{oP} \parallel r_{oN}}{1 + g_{mN}(r_{oP} \parallel r_{oN})} \approx \frac{1}{g_{mN}}$$



□ Cascode op amps

✓ 높은 gain을 위해서 differential cascode 사용



✓ Low-frequency gain

$$A_v = g_{mN} [(g_{mN} r_{oN}^2) \parallel (g_{mP} r_{oP}^2)]$$

✓ Output swing이 줄어듦

$$2[V_{DD} - (V_{OD1} + V_{OD3} + V_{CSS} + |V_{OD5}| + |V_{OD7}|)]$$

✓ pole 추가됨 → stability issue

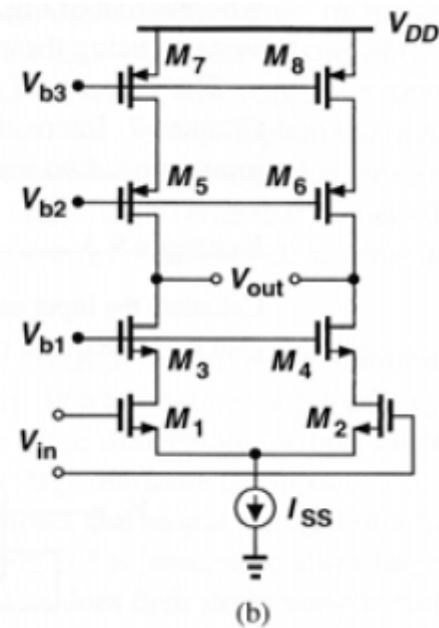 

□ Design of fully differential telescope op amp

- ✓ $V_{DD} = 3V$, differential output swing = 3V, power dissipation = 10mW, voltage gain = 2000.

$$\mu_n C_{ox} = 60 \mu A/V^2, \mu_p C_{ox} = 30 \mu A/V^2, \lambda_n = 0.1V^{-1}, \lambda_p = 0.2V^{-1}$$

$$\gamma = 0, V_{THN} = |V_{THP}| = 0.7V$$

- ✓ Power budget: $V_{DD} = 3V \rightarrow I = 3.33mA$

$$I_{M9} = 3mA, I_{Mb1} + I_{Mb2} = 330\mu A$$

- ✓ Output swing:

Node X(Y) swing = 1.5V, M_3 - M_6 in saturation.

For M_9 ,

$$|V_{OD7}| + |V_{OD5}| + V_{OD3} + V_{OD1} + V_{OD9} = 1.5V$$

Since M_9 carrying largest current,


$$V_{OD9} \approx 0.5V \text{ is chosen. } |V_{OD5}| = |V_{OD7}| \approx 0.3V,$$

$$V_{OD1} = V_{OD3} \approx 0.2V.$$

- ✓ W/L :

By $I_D = (1/2)\mu C_{ox}(W/L)(V_{GS} - V_{TH})^2$, we have
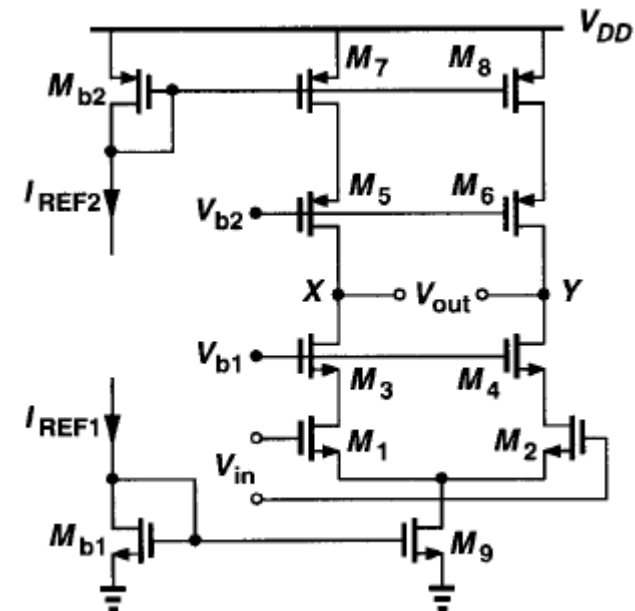
$$(W/L)_{1-4} = 1250, (W/L)_{5-8} = 1111, (W/L)_9 = 400.$$



□ Design of fully differential telescope op amp (continue)

✓ Gain:

$A_v \approx gm_1[(g_{m3}r_{o3}r_{o1}) \parallel (g_{m5}r_{o5}r_{o7})]$. In order to increase the gain,

we recognize $g_m r_o = \sqrt{2\mu C_{ox}(W/L)I_D} / (\lambda I_D) \propto \sqrt{WL/I_D}$

where $\lambda \propto 1/L$. We can therefore increase the width or length.


Choose $(W/L)_{5-8} = 1111\mu\text{m}/1\mu\text{m}$,
then $A_v \approx 4000$.

✓ CM level & bias:

Min. allowable input CM level
 $= V_{GS1} + V_{OD9} = 1.4\text{V}$.


$V_{b1, \min} = V_{GS3} + V_{OD1} + V_{OD9} = 1.6\text{V}$.

$V_{b2, \max} = V_{DD} - (|V_{GS5}| + |V_{OD7}|) = 1.7\text{V}$.

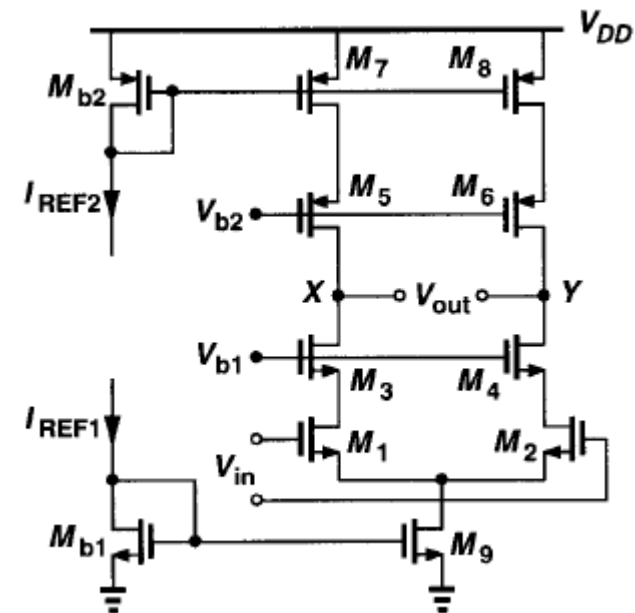


❑ Folded cascode op amps

 - ✓ telescopic cascode op amp의 단점인 제한된 output swing, input과 output을 연결하기 어려운 것 등을 Folded cascode op amp는 제거할 수 있다.



□ Folded cascode op amps (continue)

 


✓ 두 회로의 차이

In Fig.(a), one bias current, I_{SS} , provides the drain current of both the input transistors and the cascode devices.

In Fig.(b), the input pair requires an additional bias current, $I_{SS1} = I_{SS}/2 + I_{D3}$.

In Fig.(a), the input CM level cannot exceed $V_{b1} - V_{GS3} + V_{TH1}$, whereas in Fig.(b), it cannot be less than $V_{b1} - V_{GS3} + |V_{TH1}|$.

□ Folded cascode op amps (continue)

 


- ✓ Max. output voltage swing:

$$\text{Peak-peak swing} = [V_{DD} - (|V_{OD7}| + |V_{OD9}|)] - (V_{OD3} + V_{OD5}) \text{ for one side.}$$


- ✓ Swing이 telescopic Cascode 보다 커진다.
- ✓ M5와 M6 는 nodes X와 Y 의 cap 영향을 줄이기 위해서는 overdrive voltage를 사용해야 한다.

□ Folded cascode op amps (continue)


Small-signal voltage gain

 

Half circuit

 

 Equivalent circuit with output shorted to ground



Equivalent circuit with output open

$$|A_v| = G_m R_{out}$$


Since $(g_{m3} + g_{mb3})^{-1} \parallel r_{o3} \ll r_{o1} \parallel r_{o5}$, $R_{OP} \approx (g_{m7} + g_{mb7}) r_{o7} r_{o9}$
 $I_{out} \approx I_{D1}$. That is $G_m \approx g_{m1}$. $R_{out} \approx R_{OP} \parallel [(g_{m3} + g_{mb3}) r_{o3} (r_{o1} \parallel r_{o5})]$

$$\text{Thus, } |A_v| \approx g_{m1} \{ [(g_{m3} + g_{mb3}) r_{o3} (r_{o1} \parallel r_{o5})] \parallel [(g_{m7} + g_{mb7}) r_{o7} r_{o9}] \}$$


The gain is usually two or three times lower than of a comparable telescopic cascode.

□ Folded cascode op amps (continue)

 Effect of device capacitance on the nondominant pole in telescopic and folded cascode op amps



 
$$C_{tot} = C_{GS3} + C_{SB3} + C_{DB1} + C_{GD1}$$



$$C_{tot} = C_{GS3} + C_{SB3} + C_{DB1} + C_{GD1} + C_{GD5} + C_{DB5}$$

The pole at the “folding point,” i.e., the sources of M_3 and M_4 , is quite closer to the origin than that associated with the source of cascode devices in a telescopic topology.

□ A high-gain folded cascode op amp

 


The circuit provides a higher gain because of the greater mobility of NMOS devices, but at the cost of lowering the pole at the folding point,


$$\omega_{p,X} \approx (g_{m3} + g_{mb3}) / C_{tot,X}$$

□ Telescopic- vs. folded-cascode op amps: Discussion

 - ✓ folded-cascode op amp가 Telescopic-cascode op amp 보다 swing 범위가 크다는 장점을 제외하는 많은 단점을 가진다.
- ✓ 단점: higher power dissipation, lower voltage gain, lower pole frequencies, and higher noise.
- ✓ Folded-cascode op amp 가 많이 사용되는 이유는 input common-mode level을 쉽게 조절 가능하기 때문이다.



□ Design of folded-cascode op amp

 


Specifications:

$V_{DD} = 3V$, differential output swing = $3V$,

power dissipation = $10mW$, voltage gain = 2000 .

Assume $\mu_n C_{ox} = 60 \mu A/V^2$, $\mu_p C_{ox} = 30 \mu A/V^2$, $\lambda_n = 0.1V^{-1}$, $\lambda_p = 0.2V^{-1}$ (for an effective channel length of $0.5 \mu m$), $\gamma = 0$, $V_{THN} = |V_{THP}| = 0.7V$.

 - Design of folded-cascode op amp (continue)



Power budget: $I_{M11} = 1.5\text{mA}$, $I_{M9} + I_{M10} = 1.5\text{mA}$, $I_{Mb1} + I_{Mb2} + I_{Mb3} = 330\mu\text{A}$.

Output swing: one side o/p swing = 1.5V, M_3 - M_{10} in saturation.

Choose $|V_{OD5,6}| \approx 0.5V$, $|V_{OD3,4}| \approx 0.4V$, $V_{OD7,8} = V_{OD9,10} \approx 0.3V$.

W/L : By $I_D = (1/2)\mu C_{ox}(W/L)(V_{GS} - V_{TH})^2$, we have

$$(W/L)_{5.6} = 400, (W/L)_{3.4} = 313, (W/L)_{7-10} = 555.$$

O/p CM level: $CM_{min} = 0.6V$, $CM_{max} = 2.1V$, thus $CM_{opt} = 1.35V$.

□ Design of folded-cascode op amp (continue)

Determine $(W/L)_{1,2}$: min. input CM level = $V_{GS1} + V_{OD11}$.

If input and output are shorted, then $V_{GS2} + V_{OD11} = 1.35\text{V}$,

and $V_{GS1} = 0.95\text{V} \Rightarrow V_{OD1,2} = 0.25\text{V} \Rightarrow (W/L)_{1,2} = 400$.


The maximum dimensions of $M_{1,2}$ are determined by the tolerable input capacitance at nodes X and Y.

Gain: $g_m = 2I_D / (V_{GS} - V_{TH})$, we have

$g_{m1,2} = 0.006 \text{ A/V}$, $g_{m3,4} = 0.0038 \text{ A/V}$, $g_{m7,8} = 0.05 \text{ A/V}$.

For $L = x \text{ }\mu\text{m}$, find r_o .



Note $|A_v| \approx g_{m1} \{ [(g_{m3} + g_{mb3}) r_{o3} (r_{o1} \parallel r_{o5})] \parallel [(g_{m7} + g_{mb7}) r_{o7} r_{o9}] \}$

 

❑ Cascode op amps with single-ended output

Fig(a): $V_X = V_{DD} - |V_{GS5}| - |V_{GS7}|$,
limiting the maximum value of
 V_{out} to $V_{DD} - |V_{GS5}| - |V_{GS7}| -$
 $|V_{TH6}|$ and wasting one PMOS
threshold voltage in the swing.

  
Fig(b): To solve above issue, M_7 and
 M_8 are biased at the edge of
the triode region.



- swing 전압이 반으로 줄어든다.
- Node X에 pole을 가진다. → feedback speed를 제한한다.

✓ Differential 이 많이 사용된다.


9.3 Two-stage op amps

 

□ Two-stage op amp의 특징

- ✓ One stage op amp의 $\text{gain} = g_m \times R_{out} \rightarrow \text{gain} \uparrow \rightarrow \text{Cascodeing} \rightarrow \text{output swing} \downarrow$
- ✓ Output swing 을 크게 하면서 gain을 얻으려면 $\rightarrow$ Two-stage op amp $\rightarrow$ pole 수 증가 $\rightarrow$ feedback 시스템에서 stability 문제 발생
- ✓ Two-stage op amp 구성 = stage #1 (high gain) + stage #2 (high swing)

 □ Simple implementation of a two-stage op amp



Gain:


$$A_{v,1st\ stage} = g_{m1,2}(r_{o1,2} \parallel r_{o3,4})$$

$$A_{v,2nd\ stage} = g_{m5,6}(r_{o5,6} \parallel r_{o7,8})$$

$$\text{Overall gain } A_v = A_{v,1st\ stage} \times A_{v,2nd\ stage}$$

$$\text{Output swing} = V_{DD} - |V_{OD5,6}| - V_{OD7,8}$$

□ Two-stage op amp employing cascoding

 


To obtain a higher, the first stage incorporate cascode devices. The overall voltage gain is

$$A_v \approx \{g_{m1,2}[(g_{m3,4} + g_{mb3,4})r_{o3,4}r_{o1,2}] \parallel (g_{m5,6} + g_{mb5,6})r_{o5,6}r_{o7,8}]\} \times [g_{m9,10}(r_{o9,10} \parallel r_{o11,12})]$$

 9.4 Gain boosting



□ Gain boosting

- ✓ Gain을 높이는 것은 출력 저항을 높이는 것이다.
- ✓ Gain boosting 은 Cascode를 사용하지 않고 출력 저항을 높여준다.



$$R_{out} = g_{m2}r_{o2}r_{o1}$$

M_1 operates as a degeneration resistor.

 
 


$$R_{out} \approx A_1 g_{m2} r_{o2} r_{o1}$$

□ Gain boosting 증명

□ Gain boosting in cascode stage

✓ 소신호 동작에서, $V_b = 0$

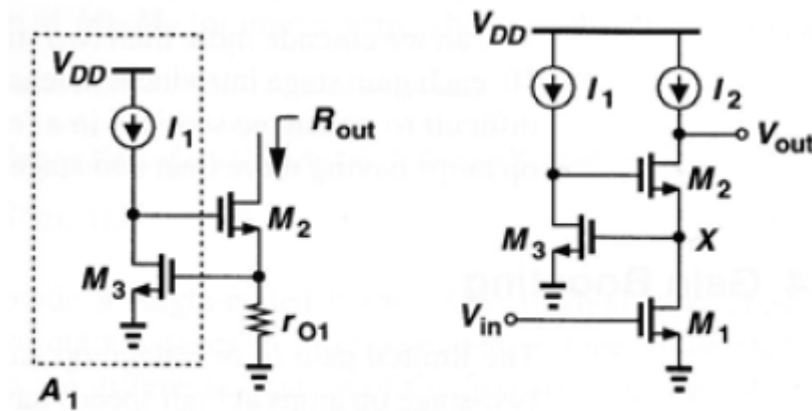 


regulated cascode

$$|A_v| \approx g_{m1} (g_{m2} r_{o2} r_{o1}) (g_{m3} r_{o3})$$

$$V_X = V_{GS3} \text{이므로,}$$


$$V_{out} \geq V_{OD2} + V_{GS3}.$$

 □ Boosting output impedance of a differential cascode stage



$$V_X = V_{GS5} + V_{ISS2} \text{ 이므로, } V_{out} \geq V_{OD3} + V_{GS5} + V_{ISS2}$$

 - ❑ Folded-cascode circuit used as auxiliary amplifier



If nodes X and Y are sensed by a PMOS pair, the minimum value of V_X and V_Y is not dictated by the gain-boosting amplifier.

The minimum allowable level of V_x and V_y is given by $V_{OD1,2} + V_{ISS1}$.

Output impedance: Since $\frac{V_P}{V_X} = g_{m5}R_{out1}$

where $R_{out1} \approx [g_{m7}r_{o7}(r_{o9}||r_{o5})] || (g_{m11}r_{o11}r_{o13})$, $R_{out} \approx g_{m3}r_{o3}r_{o1}g_{m5}R_{out1}$.

9.5 Comparison of various op amps

	Gain	Output Swing	Speed	Power Dissipation	Noise
Telescopic	Medium	Medium	Highest	Low	Low
Folded-Cascode	Medium	Medium	High	Medium	Medium
Two-stage	High	Highest	Low	Medium	Low
Gain-Boosted	High	Medium	Medium	High	Medium

8.6 Common-mode feedback (CMFB)


□ Full differential circuits의 single-ended circuits에 대한 장점

- ✓ output swings 증가
- ✓ mirror poles 피할 수 있어서 higher closed-loop speed


□ 그러나, high-gain differential circuits 은 common-mode feedback.

□ Simple differential pair (입력과 출력을 short 시킴)

 - ✓ Input & output common-mode level $\rightarrow V_{DD} - I_{SS} R_D / 2$



 □ High-gain differential pair (입력과 출력을 short 시킴)



□ nodes X and Y 에서의 common-mode level ?


- ✓ 입력 TR M1, M2가 전류 $I_{SS}/2$ 를 통과시킨다면, CM level 은 I_{D3} 와 I_{D4} 가 얼마나 같은가에 의하여 결정된다.

□ Effect of current mismatches: Mismatches in PMOS and NMOS current mirrors

- ✓ current mirror $\rightarrow I_{D5} = I_{SS}$ & $I_{D3,4} = I_{SS}/2$.
- ✓ If $I_{D3,4} > I_{SS}/2$, $\rightarrow$ M3와 M4 는 triode region $\rightarrow$ drain currents fall to $I_{SS}/2$.
- ✓ If $I_{D3,4} < I_{SS}/2$, $\rightarrow V_X$ 와 V_Y 는 낮아짐 $\rightarrow$ M5는 triode region $\rightarrow$ M5의 전류 $2 \times I_{D3,4}$.

□ Simplified model of high-gain amplifier

 
✓ high-gain amplifiers에서 p-type / n-type 전류를 정확하게 맞추어야 한다.



$$\Delta V = (I_P - I_N)(R_P \parallel R_N)$$


✓ Mismatch $\rightarrow$ current error 발생 $\rightarrow R_P \parallel R_N$ 이 큼 $\rightarrow$ voltage error 이 커짐 $\rightarrow$ p-type / n-type current source 가 triode region

□ Conceptual topology for CMFB.

 


- ✓ high-gain amplifiers 에서 output CM level 은 공정 특성과 mismatch에 민감 하지만 differential feedback 으로는 안정화 시키기 어렵다.
- ✓ CMFB network = 두 출력의 CM level을 감지 → bias current 중 하나를 조정

□ CMFB with resistive sensing

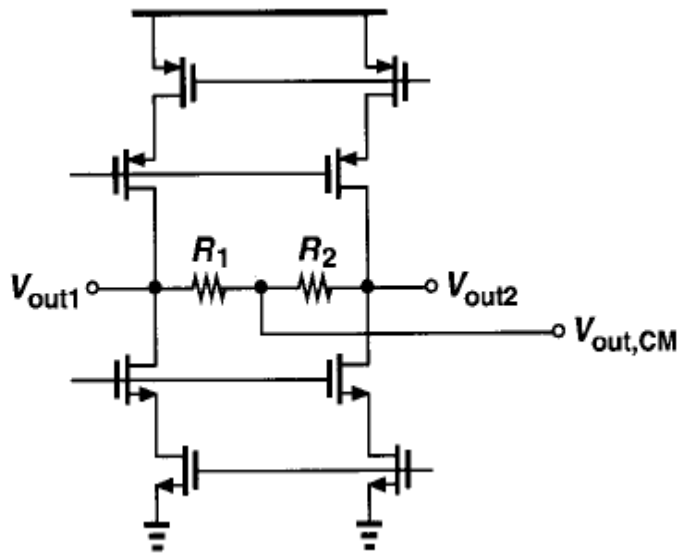

- ✓ Output CM level $\rightarrow V_{out,CM} = (V_{out1} + V_{out2})/2$
- ✓ Resistive divider level
 $\rightarrow V_{out,CM} = (R_1 V_{out2} + R_2 V_{out1})/(R_1 + R_2) \rightarrow (V_{out1} + V_{out2})/2$, if $R_1 = R_2$.
- ✓ R_1 과 R_2 는 open-loop gain에 영향을 주지 않기 위해서 출력 저항보다 커야 한다.


□ CMFB using source followers

 

□ output CM level이 $V_{GS7,8}$ 만큼 줄지만 보상에서 고려되기 때문에 상관없다.


✓ $R1, R2, I1, I2$ 큰 출력을 영향 주지 않을 만큼은 커야 한다.

□CMFB using source followers

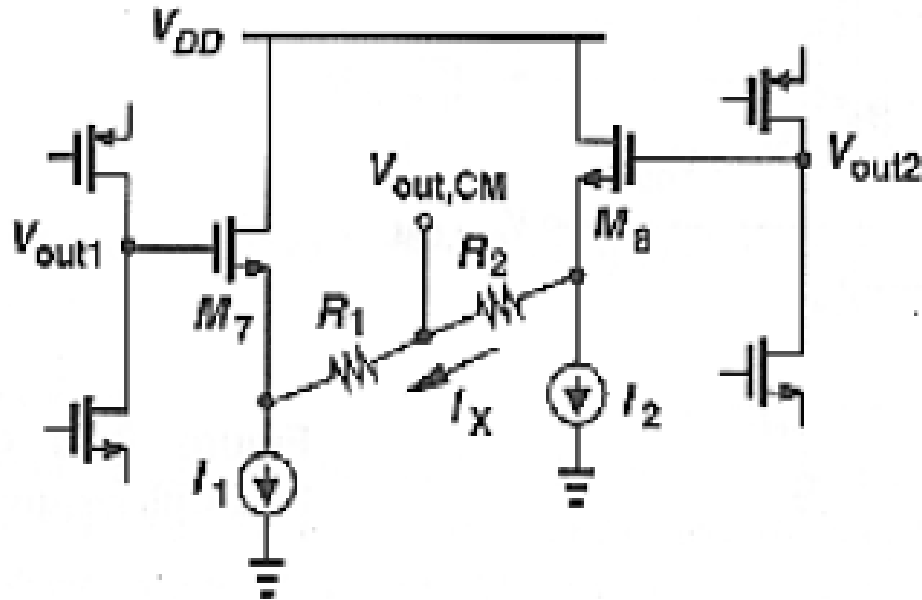


- ✓ If $V_{out2} \gg V_{out1}$, I_1 에 모든 전류가 흐른다.
- ✓ $I_X \approx (V_{out2} - V_{out1}) / (R_1 + R_2)$
- ✓ $(R_1 + R_2)$ 또는 I_1 이 충분히 크지 못하면 $\rightarrow I_{D7} \sim 0 \rightarrow V_{out,CM}$ 이 output CM level 을 반영하지 못한다.

 □ Sensing and controlling output CM level




 Alternative method of controlling output CM level



 9.7 Input range limitations


□ Differential input swing은 보통 매우 작지만, unit-gain buffer의 경우 넓은 input swing 을 필요로 한다.




✓ $V_{in,min} \approx V_{out,min} = V_{GS1,2} + V_{ISS}$.

✓ If $V_{in} < V_{in,min} \rightarrow$ MOS transistor (I_{SS}) enters triode region $\rightarrow$ bias current $\downarrow \rightarrow$ transconductance $\downarrow$

□ Extension of input CM range

 


 Variation of equivalent transconductance with the input CM level.



 9.8 Slew rate

□ Response of a linear circuit to input step



□ dV_{out}/dt : Since $V_{out} = V_0[1 - \exp(-t/\tau)]$, where $\tau = RC$, we have

$$\frac{dV_{out}}{dt} = \frac{V_0}{\tau} \exp \frac{-t}{\tau}$$

□ $dV_{out}/dt \propto V_0$; if we apply a larger input step, the output rises more rapidly.

□ Response of a linear op amp to step response

□ Assume op amp is linear,

$$\left[\left(V_{in} - V_{out} \frac{R_2}{R_1 + R_2} \right) A - V_{out} \right] \frac{1}{R_{out}} = \frac{V_{out}}{R_1 + R_2} + V_{out} C_L s$$


Assume $R_1 + R_2 \gg R_{out}$, we have

$$\frac{V_{out}}{V_{in}}(s) \approx \frac{A}{\left(1 + A \frac{R_2}{R_1 + R_2} \right) \left[1 + \frac{R_{out} C_L}{1 + A R_2 / (R_1 + R_2)} s \right]}$$

The step response is given by


$$V_{out} = V_0 \frac{A}{1 + A \frac{R_2}{R_1 + R_2}} \left(1 - \exp \frac{-t}{\frac{C_L R_{out}}{1 + A R_2 / (R_1 + R_2)}} \right) u(t)$$

 indicating that the slope is proportional to the final value.
This type of response is called “linear settling.”




❑ Slewing in an op amp circuit

 - ✓ 작은 입력 신호에는 exponential 함수로 증가하지만 큰 입력 신호에서는 선형적으로 증가한다.




$$V_{out} = V_0 \frac{A}{1 + A \frac{R_2}{R_1 + R_2}} \left(1 - \exp \frac{-t}{\frac{C_L R_{out}}{1 + A R_2 / (R_1 + R_2)}} \right) u(t) \quad \dots\dots(A)$$

 
□ Small-signal operation of a simple op amp




 
□ Small-signal operation of a simple op amp



 □ Small-signal operation of a simple op amp



□ Slewing in telescopic op amp

  

V_{out1} and V_{out2} appear as ramps with slopes equal to $\pm I_{SS} / (2C_L)$, and consequently $V_{out1} - V_{out2}$ exhibits a slew rate equal to I_{SS} / C_L .

❑ Slewing in folded-cascode op amp

- If $I_P \geq I_{SS}$, the slew rate is equal to I_{SS}/C_L , independent of I_P .

