
 


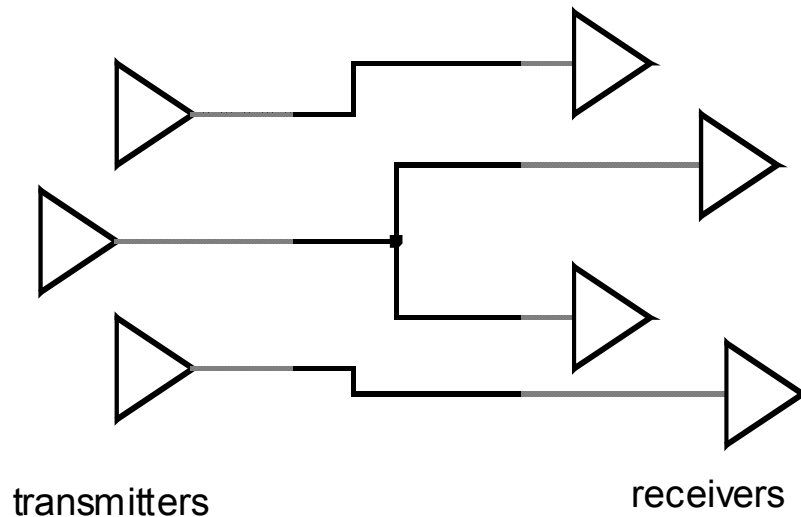


Digital Integrated Circuits

The Wire

The Wire



schematics

 

physical


Wire?

→ metal line / poly silicon / n^+ p^+ diffusion layer → delay / power / noise (reliability)


Include all parasitic effect ?

→ Not feasible for millions of circuit nodes → circuit behavior is only determined by a few dominant parameter → clear insight into the parasitic wiring effects


Interconnect Impact on Chip

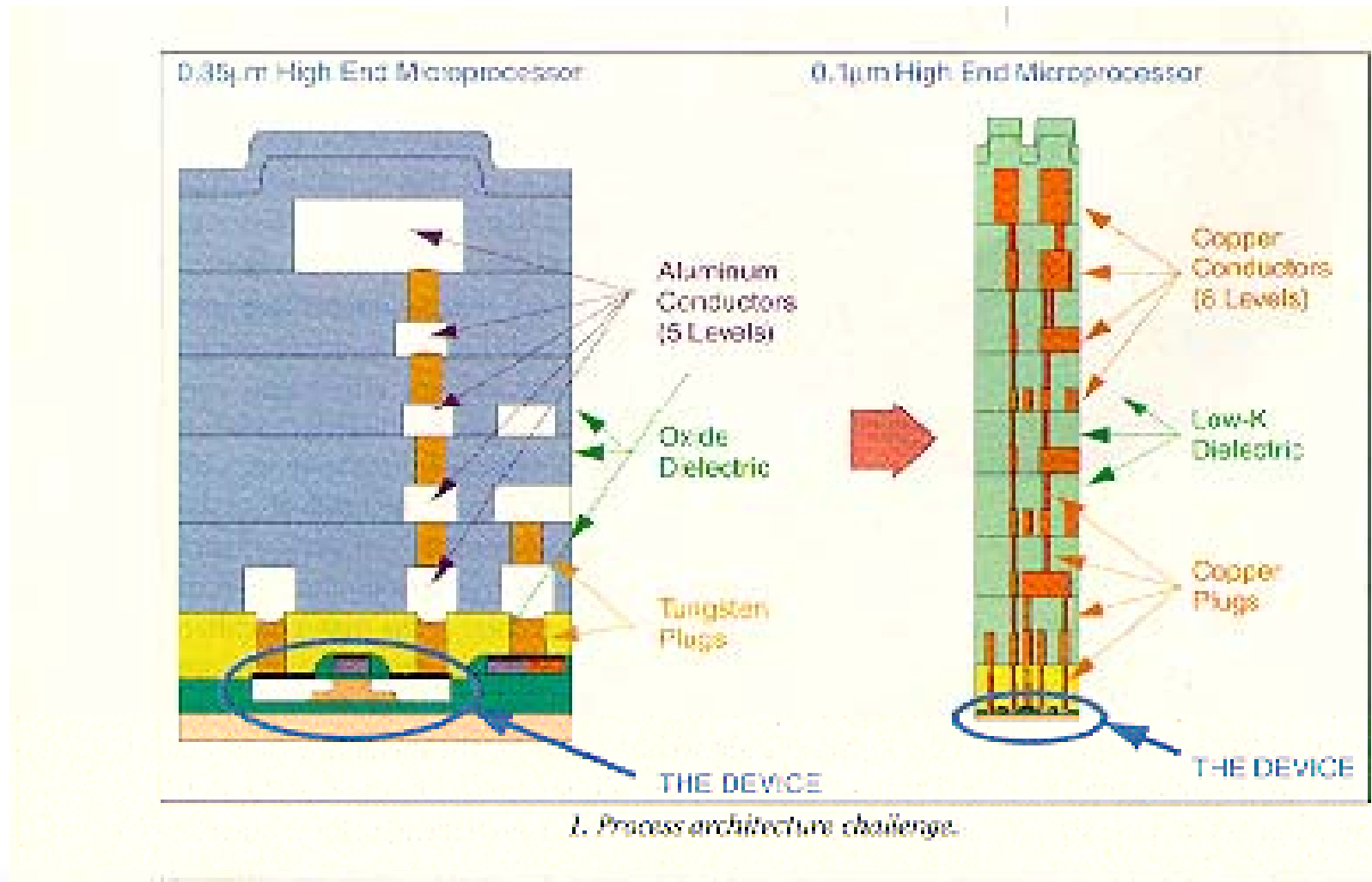

Wire Models

 

All-inclusive model

 

Capacitance-only

R, L, C

→ R, C when $R \uparrow$ or $T_{\text{rise}}/T_{\text{fall}}$ is slow

→ C only when wire is short or $R \downarrow$

→ Inter-wire C is ignored when space between wires is large


Impact of Interconnect Parasitics

❑ Interconnect parasitics


- reduce reliability
- affect performance and power consumption

❑ Classes of parasitics

- Capacitive
- Resistive
- Inductive

 


Nature of Interconnect

 


Source: Intel

INTERCONNECT


Capacitance

 

Capacitance of Wire Interconnect

 


Capacitance: The Parallel Plate Model

 


$$C_{int} = \frac{\epsilon_{di}}{t_{di}} WL$$

$$S_{Cwire} = \frac{S}{S \cdot S_L} = \frac{1}{S_L}$$

Fringing Capacitance

 


(a)

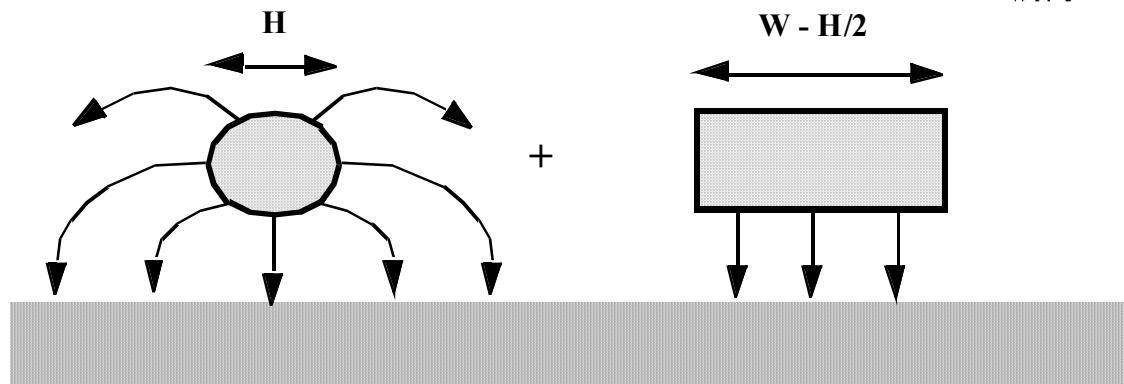

(b)


$$c_{wire} = c_{pp} + c_{fringe} = \frac{w\epsilon_{di}}{t_{di}} + \frac{2\pi\epsilon_{di}}{\log(t_{di}/H)}$$

Fringing versus Parallel Plate

 


(from [Bakoglu89])

Interwire Capacitance

 

Impact of Interwire Capacitance

 

(from [Bakoglu89])

Wiring Capacitances (0.25 μm CMOS)

	Field	Active	Poly	Al1	Al2	Al3	Al4
Poly	88						
	54						
Al1	30	41	57				
	40	47	54				
Al2	13	15	17	36			
	25	27	29	45			
Al3	8.9	9.4	10	15	41		
	18	19	20	27	49		
Al4	6.5	6.8	7	8.9	15	35	
	14	15	15	18	27	45	
Al5	5.2	5.4	5.4	6.6	9.1	14	38
	12	12	12	14	19	27	52


Capacitance of Metal Wire

□ Example


- Al1 layer L=10cm W=1um
- Total capacitance?
- Total capacitance = 11pF
 - Area cap = $(0.1 \times 10^6 \text{um}^2) \times 30 \text{aF/um}^2 = 3 \text{pF}$
 - Fringing cap = $2 \times (0.1 \times 10^6 \text{um}^2) \times 40 \text{aF/um}^2 = 8 \text{pF}$

INTERCONNECT

Resistance

 


Wire Resistance

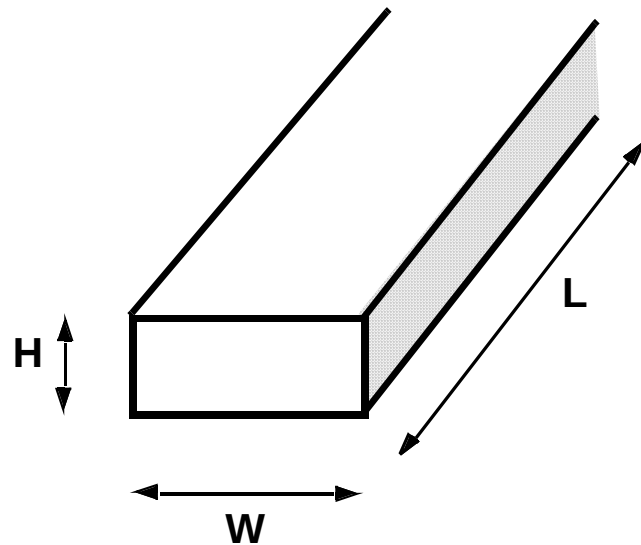

$$R = \frac{\rho L}{HW}$$

Sheet Resistance
 R_0

 

Resistance of Metal Wire

□ Example

- Al1 layer $L=10\text{cm}$ $W=1\mu\text{m}$, sheet $R = 0.075\Omega/\square$
- Polysilicon $L=10\text{cm}$ $W=1\mu\text{m}$, sheet $R = 175\Omega/\square$
- Total Resistance ?
- Total Resistance
 - Al $\rightarrow R_{\text{wire}} = 0.075\Omega/\square \times (0.1 \times 10^6 \mu\text{m}^2) / 1\mu\text{m} = 7.5\text{K}\Omega$
 - Polysilicon $\rightarrow R_{\text{wire}} = 175\Omega/\square \times (0.1 \times 10^6 \mu\text{m}^2) / 1\mu\text{m} = 17.5\text{M}\Omega$


Interconnect Resistance

Material	ρ ($\Omega\text{-m}$)
Silver (Ag)	1.6×10^{-8}
Copper (Cu)	1.7×10^{-8}
Gold (Au)	2.2×10^{-8}
Aluminum (Al)	2.7×10^{-8}
Tungsten (W)	5.5×10^{-8}

Dealing with Resistance

- ❑ **Selective Technology Scaling**
- ❑ **Use Better Interconnect Materials**
 - reduce average wire-length
 - e.g. copper, silicides
- ❑ **More Interconnect Layers**
 - reduce average wire-length

Polycide Gate MOSFET

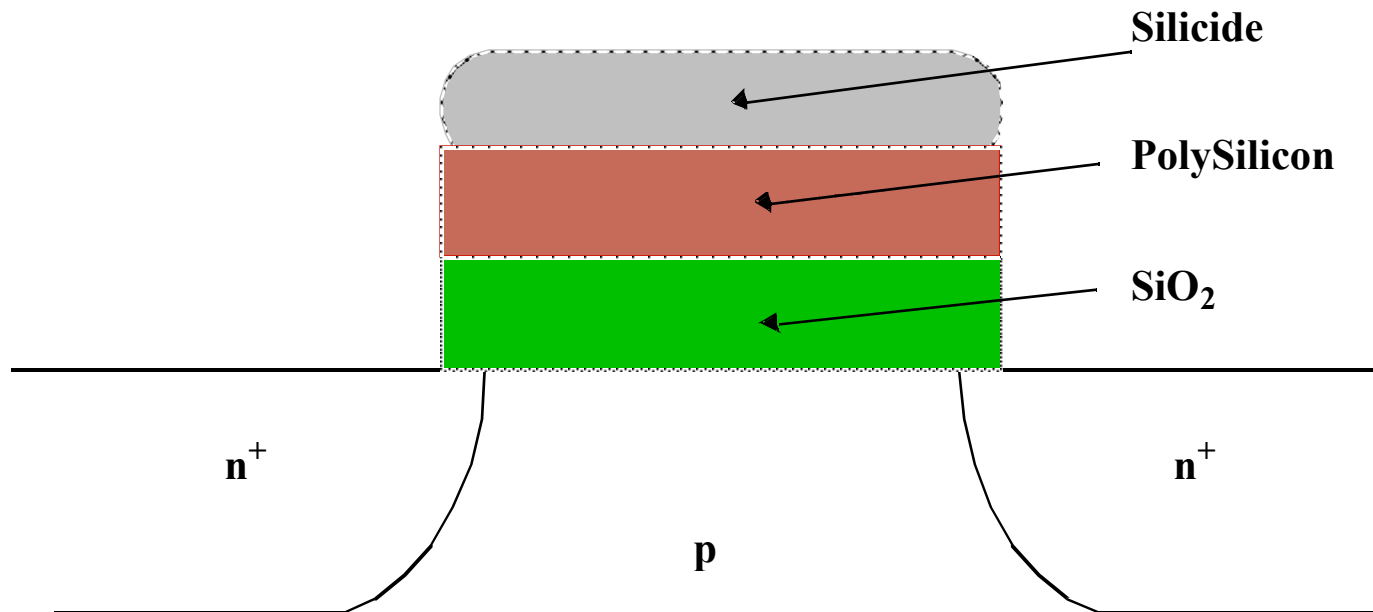


Silicides: WSi₂, TiSi₂, PtSi₂ and TaSi

Conductivity: 8-10 times better than Poly

Sheet Resistance

Material	Sheet Resistance ($\Omega/\square$)
n- or p-well diffusion	1000 – 1500
n^+ , p^+ diffusion	50 – 150
n^+ , p^+ diffusion with silicide	3 – 5
n^+ , p^+ polysilicon	150 – 200
n^+ , p^+ polysilicon with silicide	4 – 5
Aluminum	0.05 – 0.1

Modern Interconnect

 


Example: Intel 0.25 micron Process

5 metal layers
Ti/Al - Cu/Ti/TiN
Polysilicon dielectric


<u>LAYER</u>	<u>PITCH</u>	<u>THICK</u>	<u>A.R.</u>
Isolation	0.67	0.40	-
Polysilicon	0.64	0.25	-
Metal 1	0.64	0.48	1.5
Metal 2	0.93	0.90	1.9
Metal 3	0.93	0.90	1.9
Metal 4	1.60	1.33	1.7
Metal 5	2.56	1.90	1.5
	μm	μm	

Layer pitch, thickness and aspect ratio

 

INTERCONNECT

Inductance

 

Inductance

□ $\Delta V = L \, di/dt \rightarrow L?$

□ $CL = \epsilon\mu$

▪ $\leftarrow$ Maxwell's law

$$v = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\epsilon\mu}} = \frac{C_0}{\sqrt{\epsilon_r \mu_r}}$$

Inductance of Metal Wire

□ Example




- $C = (W \times 30 + 2 \times 40) \text{ aF}/\mu\text{m}$
- $L = \epsilon\mu / C = (3.9 \times 8.854 \times 10^{-12}) \times (4\pi \times 10^{-7}) / C$
 - $W = 0.4 \mu\text{m}$ $C = 92 \text{ aF}/\mu\text{m}$ $L = 0.47 \text{ pH}/\mu\text{m}$
 - $W = 1 \mu\text{m}$ $C = 110 \text{ aF}/\mu\text{m}$ $L = 0.39 \text{ pH}/\mu\text{m}$
 - $W = 10 \mu\text{m}$ $C = 380 \text{ aF}/\mu\text{m}$ $L = 0.11 \text{ pH}/\mu\text{m}$
- $R = 0.075/W \text{ } \Omega/\mu\text{m}$
- $\omega L = R \text{ ? } \rightarrow 30.6 \text{ GHz for } W = 1 \mu\text{m}$



Interconnect Modeling

The Lumped Model

Simple but effective for digital IC

 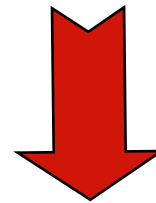 


Lumped Model of Metal Wire

□ Example

- Al1 layer $L=10\text{cm}$ $W=1\mu\text{m}$ $\rightarrow C_{\text{lumped}} = 11\text{pF}$
- $R_{\text{driver}} = 10\text{K}\Omega$
- $V_{\text{out}}(t) = (1 - e^{-t/\tau})V$
 - $\tau = R_{\text{driver}} \times C_{\text{lumped}} = 10\text{K}\Omega \times 11\text{pF}$
 - 50% $\rightarrow t = \ln(2) \tau = 0.69 \tau = 76\text{ns}$
 - 90% $\rightarrow t = \ln(9) \tau = 2.2 \tau = 242\text{ns}$


Lumped RC-Model (Elmore Delay)

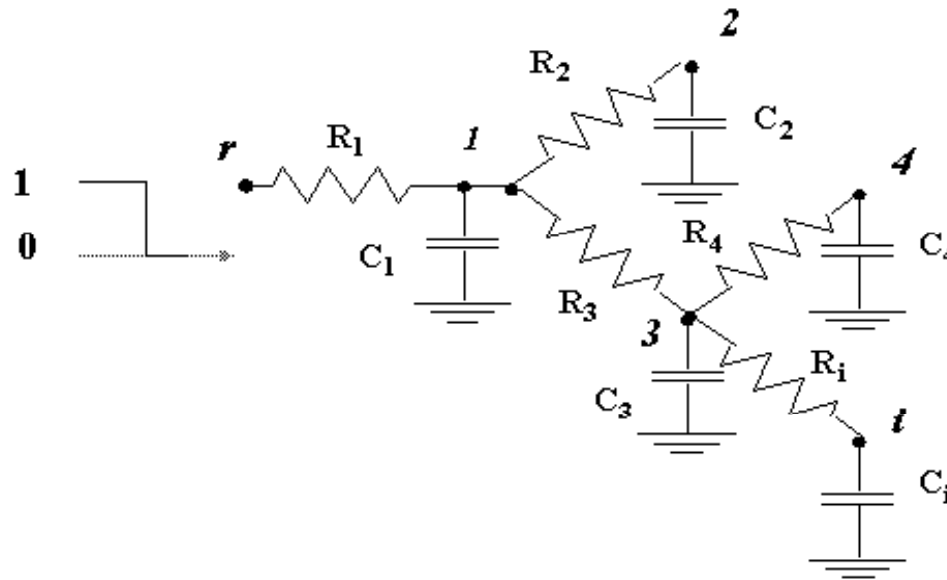

$$R_{ik} = \sum_N R_j \Rightarrow (R_j \in [path(s \rightarrow i) \cap path(s \rightarrow k)])$$

$$\tau_{Di} = \sum_{k=1} C_k R_{ik}$$

The Elmore Delay - RC Chain

 

$$\tau_N = \sum_{i=1}^N R_i \sum_{j=i}^N C_j = \sum_{i=1}^N C_i \sum_{j=1}^i R_j$$

Wire Model


Assume: Wire modeled by N equal-length segments

$$\tau_{DN} = \left(\frac{L}{N}\right)^2 (rc + 2rc + \dots + Nrc) = (rcL^2) \frac{N(N+1)}{2N^2} = RC \frac{N+1}{2N}$$

For large values of N:

$$\tau_{DN} = \frac{RC}{2} = \frac{rcL^2}{2}$$

The Distributed RC-line

 


$$rc \frac{\partial V}{\partial t} = \frac{\partial^2 V}{\partial x^2}$$

The diffusion equation

$$\tau(V_{out}) = \frac{rc L^2}{2}$$

 
Step-response of RC wire as a function of time and space




RC-Models

Voltage Range	Lumped RC-network	Distributed RC-network
0→50% (t_p)	0.69 RC	0.38 RC
0→63% (τ)	RC	0.5 RC
10%→90% (t_T)	2.2 RC	0.9 RC

 Step Response of Lumped and Distributed RC Networks:
Points of Interest.



Driving an RC-line

 

$$\tau_D = R_s C_w + \frac{R_w C_w}{2} = R_s C_w + 0.5 r_w c_w L^2$$

$$t_p = 0.69 R_s C_w + 0.38 R_w C_w$$

Design Rules of Thumb

- rc delays should only be considered when $t_{pRC} \gg t_{pgate}$ of the driving gate

$$L_{crit} \gg \sqrt{t_{pgate}/0.38rc}$$

- rc delays should only be considered when the rise (fall) time at the line input is smaller than RC, the rise (fall) time of the line

$$t_{rise} < RC$$

- when not met, the change in the signal is slower than the propagation delay of the wire